

Instrumentation and Control

AIAC 012 008

012 Install and service electrical and electronic equipment
 008 Assemble electrical components and appliances

Assessment Tool

Learner Name:		Signed:	
Telephone No.:		Date:	
Marks:	Maximal total marks		
	Obtained marks		
	Total obtained marks in percentage	%	
Learner Is:	<input type="checkbox"/> Competent <input type="checkbox"/> Not Yet Competent		
Occupation Safety and Health Considerations	Follow Health, Safety and Environment ACT 2007 of Kenya.		
Instructor Name:		Signed:	

Assignment

Task: IAC 012, Element 8: Assemble electrical components and appliances	Duration : 12 hours
Job Statement	Electrical components functions and appliances of the Siemens LOGO! Controller
Performance Criteria	<ul style="list-style-type: none">• Identification of components and appliances• Constructional features, principles of operation and functions of components and appliances• Analysis connecting points and joints• Selection of components and appliances
Resources Required	List of Recommended Resources <ul style="list-style-type: none">• User Manual Siemens LOGO! https://cache.industry.siemens.com/dl/files/461/16527461/att_82564/v1/Logo_e.pdf• Siemens Online E-Learning https://sitrain.automation.siemens.com/sitrain/open_wbt/logo/tutorial/menu.html?mode=standalone
Name of Developer	Dr. Lawrence Mukhongo, TUM, June 2017

Overview of LOGO! Functions

LOGO! provides you with various elements in programming mode. In order to maintain the overview, we have organized the elements in 'Lists'. These lists are:


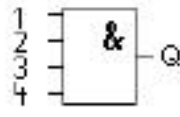
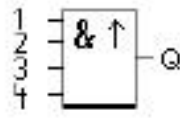
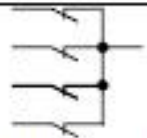
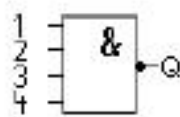
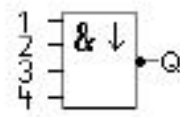
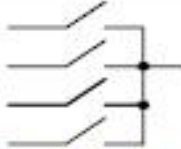
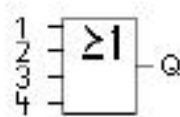

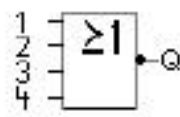

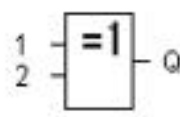
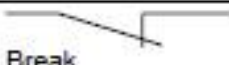
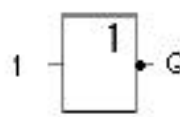
- ↓Co: Connectors
Connectors represent inputs (I1, I2 ...), outputs (Q1, Q2 ...), flags and constant voltage levels (constants).
- ↓GF: Basic functions AND, OR,
The GF list contains the basic function blocks you can use for your circuit program. Basic functions represent simple logical elements of Boolean algebra. You can invert the inputs of individual basic functions, that is, the circuit program inverts a logical "1" at a relevant input to a logical "0"; if "0" is set at the input, the program sets a logical "1" ..
- ↓SF: Special functions
Because of their different input designation, there is a difference between the special functions and basic functions. SFs contain timer functions, retentive functions and various parameter assignment options, which allow you to adapt the circuit program to suit your own requirements.
- ↓BN: Reusable blocks configured in the circuit program

If LOGO! does not show all elements:

- No further blocks may be added. This is either an indication of insufficient memory space or that the maximum number of blocks has been reached.
- A specific block's memory space requirement would exceed the space available in LOGO!

Learning Material

Overview Basic functions -- GF

View in the circuit diagram	View in LOGO!	Name of the basic function
 <p>Series circuit make contact</p>		AND (see page 106)
		AND with edge evaluation (see page 106)
 <p>Parallel circuit with break contacts</p>		NAND (not AND) (see page 107)
		NAND with edge evaluation (see page 108)
 <p>Parallel circuit with make contacts</p>		OR (see page 109)
 <p>Series circuit with break contacts</p>		NOR (not OR) (see page 109)
 <p>Double changeover contact</p>		XOR (exclusive OR) (see page 110)
 <p>Break contact</p>		NOT (negation, inverter) (see page 111)

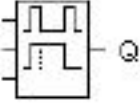
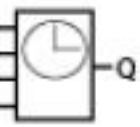
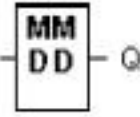
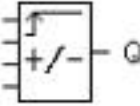
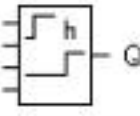

Learning Material

Overview Special functions – SF (page 1)

View in LOGO!	Name of the special function	Rem
Times		
	On-delay (see page 120)	REM
	Off-delay (see page 123)	REM
	On-/Off-delay (see Page 124)	REM
	Retentive on-delay (see page 126)	REM
	Wiping relay (pulse output) (see page 127)	REM
	Edge triggered wiping relay (see page 128)	REM
	Asynchronous pulse generator (see Page 130)	REM
	Random generator (see page 132)	
	Stairway lighting switch (see page 134)	REM

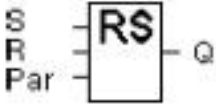
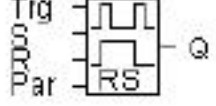

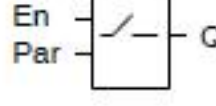
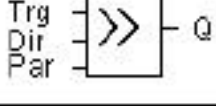
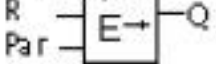
Learning Material

Overview Special functions – SF (page 2)

View in LOGO!	Name of the special function	Rem
Trg R Par 	Multiple function switch (see page 136)	REM
No1 No2 No3 Par 	Weekly timer (see Page 139)	
No 	Yearly timer (see Page 143)	
Counter		
R Cnt Dir Par 	Up/down counter (see Page 149)	REM
R En Ral Par 	Hours counter (see page 152)	REM
Fre Par 	Threshold trigger (see Page 156)	

Learning Material

Overview Special functions – SF (page 3)

	<p>Latching relay (see Page 174)</p>	<p>REM</p>
	<p>Pulse relay (see Page 175)</p>	<p>REM</p>
	<p>Message texts (see Page 177)</p>	
	<p>Softkey (see Page 189)</p>	<p>REM</p>
	<p>Shift register (see Page 192)</p>	<p>REM</p>
	<p>Analog math error detection (see Page 212)</p>	


Practical Assessment:

Task 1:

Match the designations

- Functions Block
- Ladder Diagram







to the circuit diagrams below

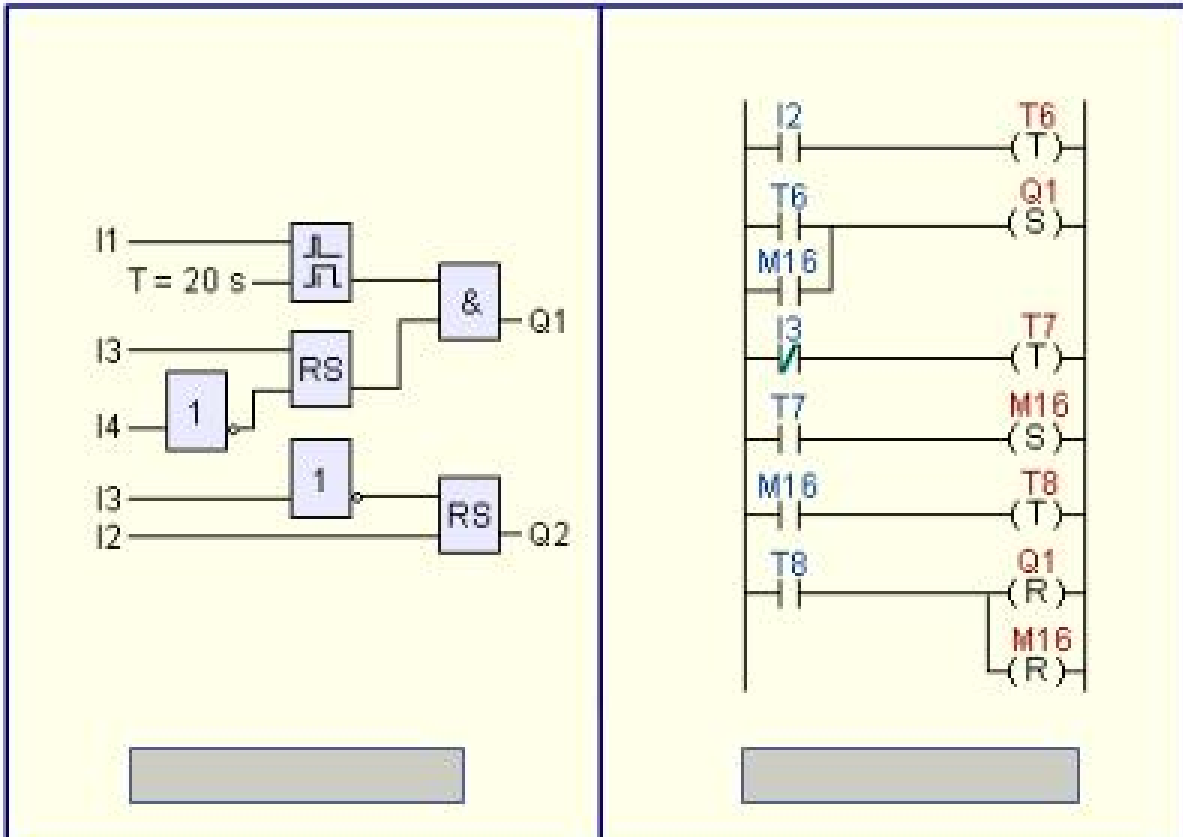

Practical Assessment:

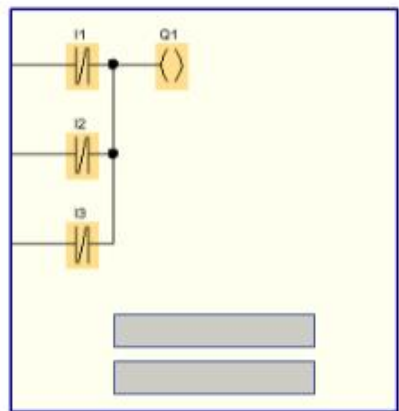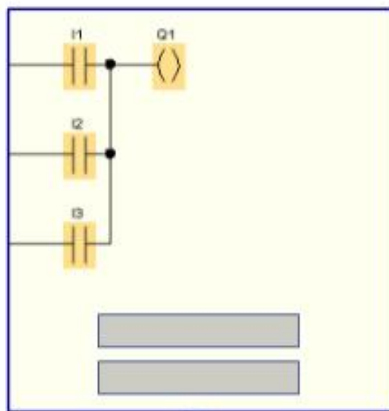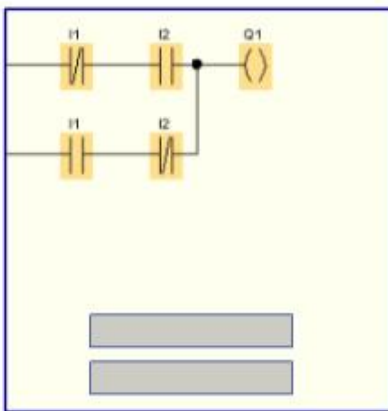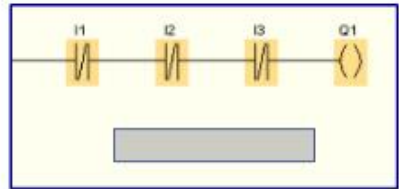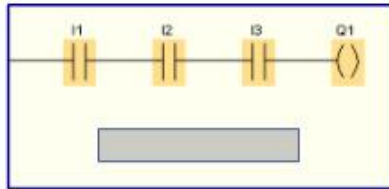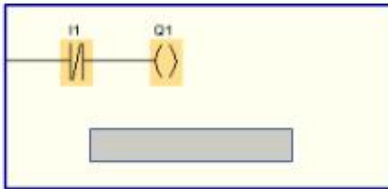Task 2:

Below you can see some basic circuits in ladder diagram view. Assign the appropriate function equations to the ladder diagrams. Several solutions may be possible, but this is not imperative.



$$Q_1 = \overline{I_1} + \overline{I_2} + \overline{I_3}$$

$$Q_1 = I_1 \cdot I_2 \cdot I_3$$

$$Q_1 = \overline{I_1} \cdot \overline{I_2} \cdot \overline{I_3}$$

$$Q_1 = (I_1 \cdot \overline{I_2}) + (\overline{I_1} \cdot I_2)$$

$$Q_1 = \overline{I_1}$$

$$Q_1 = \overline{I_1} \cdot I_2 \cdot I_3$$

$$Q_1 = \overline{I_1 + I_2} \cdot I_3$$


$$Q_1 = \overline{\overline{I_1} \cdot \overline{I_2} \cdot \overline{I_3}}$$

$$Q_1 = I_1 + I_2 + I_3$$


Practical Assessment

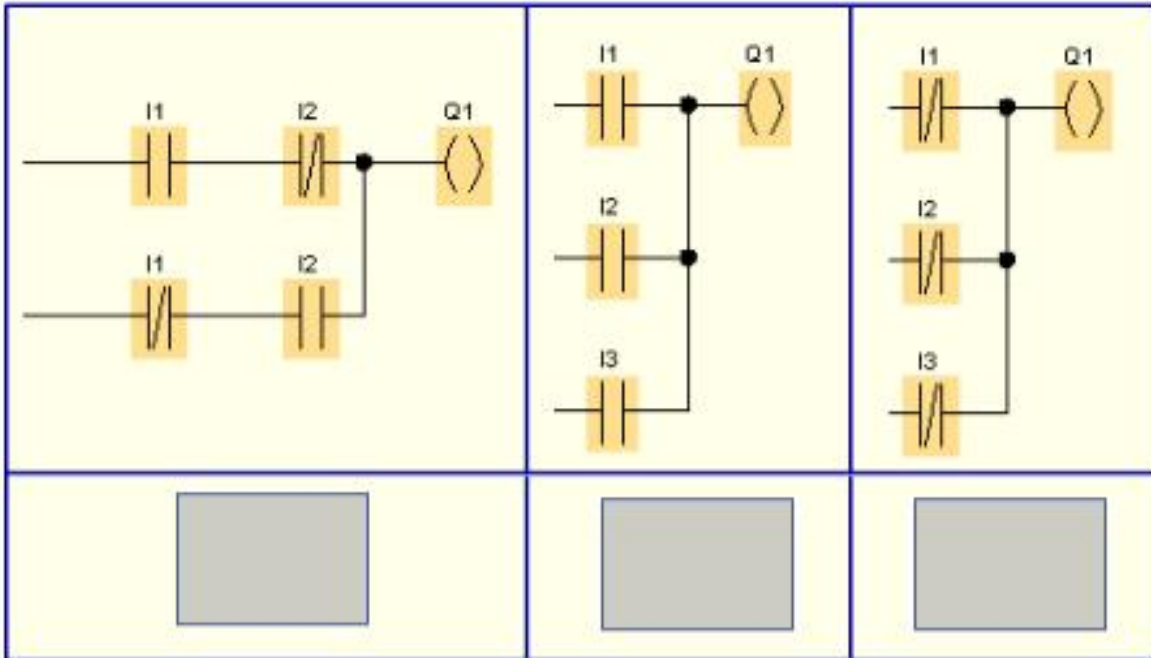Task 3:

Below you can see some basic circuits in ladder diagram view. Assign the appropriate function to the ladder diagrams.




Functions:

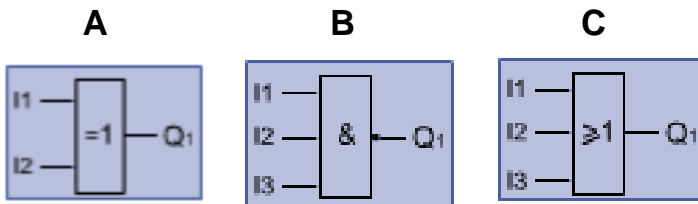

Practical Assessment

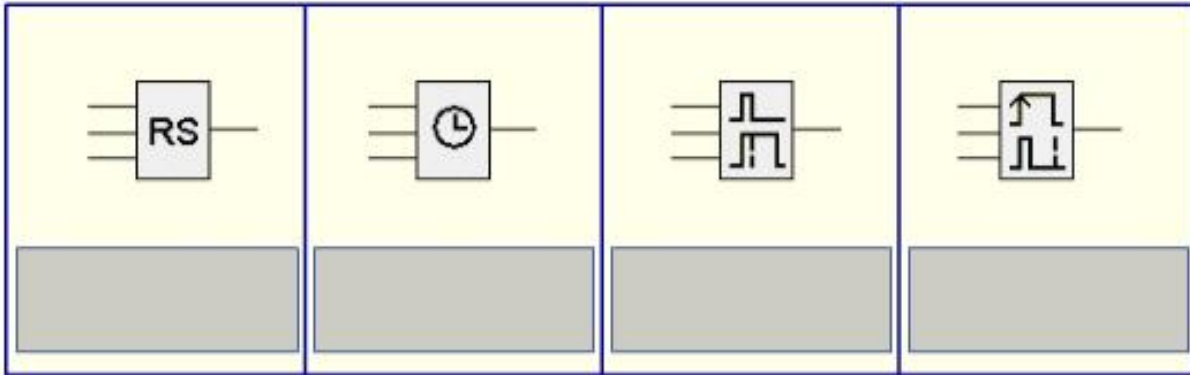Task 4:

Assign the appropriate function designation to the views.



Functions:

A

Flank triggered
Interval time delay relay

B

Switch off delay

C

Lock up relay


D

Weekly time switch

Practical Assessment

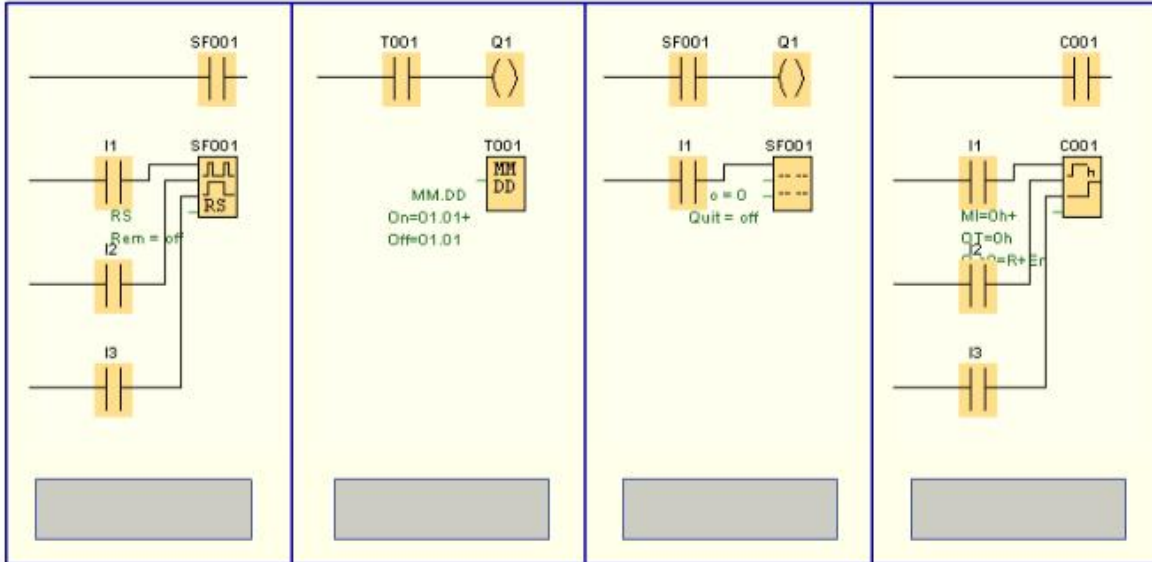Task 5:

Assign the appropriate function designation to the views.




Functions:

- A Message text
- B Annual time switch
- C Operating hours
- D Current surge relay

Practical Assessment

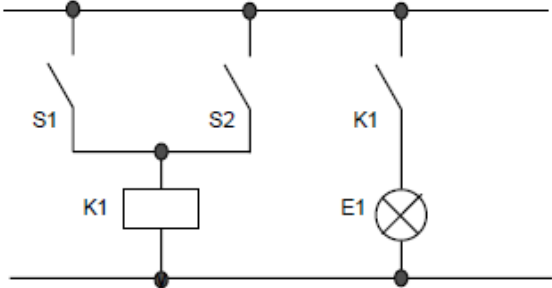Task 6:

Below you will see a circuit diagram. Find the LOGO solution and create for this circuit the functions block diagram.



Practical Assessment

Task 7:

A bottle filling machine is to be controlled. The conveyor control is switched ON or OFF using (I1). When the conveyor control is switched ON, the motor for the conveyor belt (Q1) runs. The motor is able to be switched off at any time with an Emergency switch (I3)

Find the LOGO solution and create for this requirement

- a) The circuit diagram and
- b) The functions block diagram.


Assessment Checklist

Learner ID and Name:			
Assessment	AIAC 012 008 SAC Functions	Date:	







Items to be Evaluated	Tolerance	C	NYC
The student knows functions blocks and ladder diagrams (Task 1)			
The student assigns the appropriate function equations to ladder diagrams. (Task 2 – 5)			
The student converts circuit diagrams into LOGO function blocks (Task 6)			
The student is able to find a solution for different requirement of industrial, applications and is able to create function diagrams (Task 7)			
Remarks			
Learner is	<input type="checkbox"/> Competent <input type="checkbox"/> Not Yet Competent		
Occupation Safety and Health Considerations	Follow Health, Safety and Environment ACT 2007 of Kenya.		
Name and Signature of Instructor/Assessor			

Sample Answers - Practical Assessment:

Task 1:

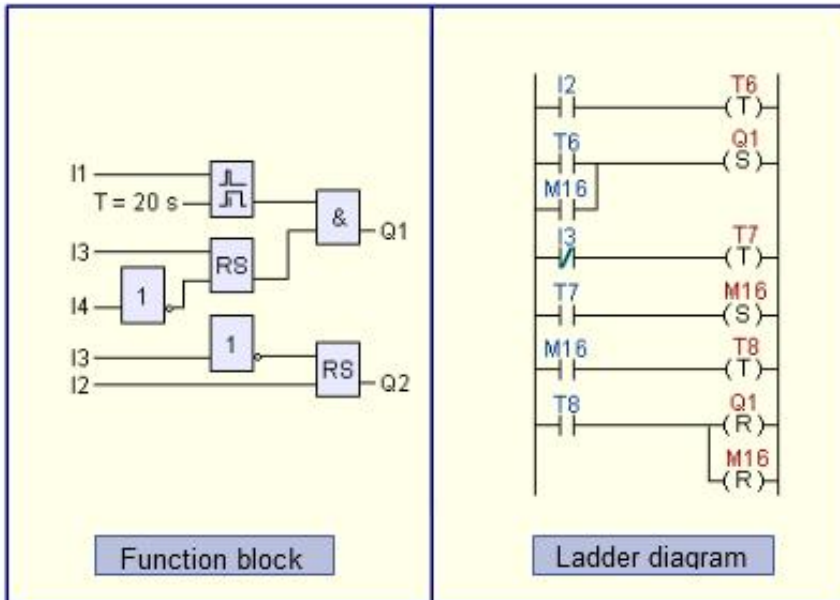


Task 2

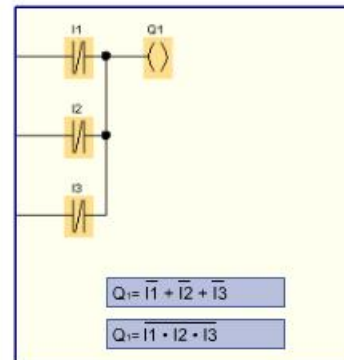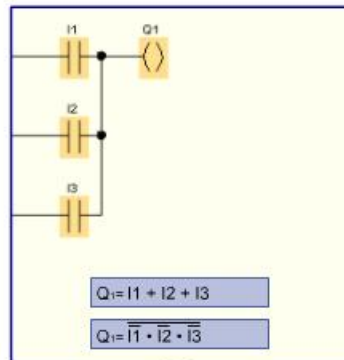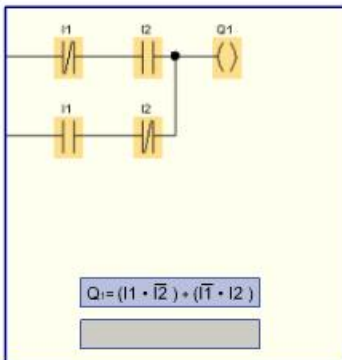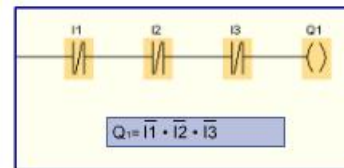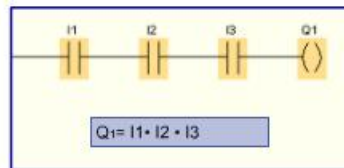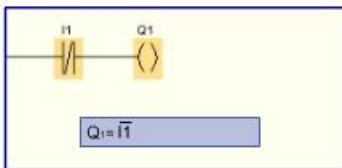


Sample Answers - Practical Assessment:


Task 3:

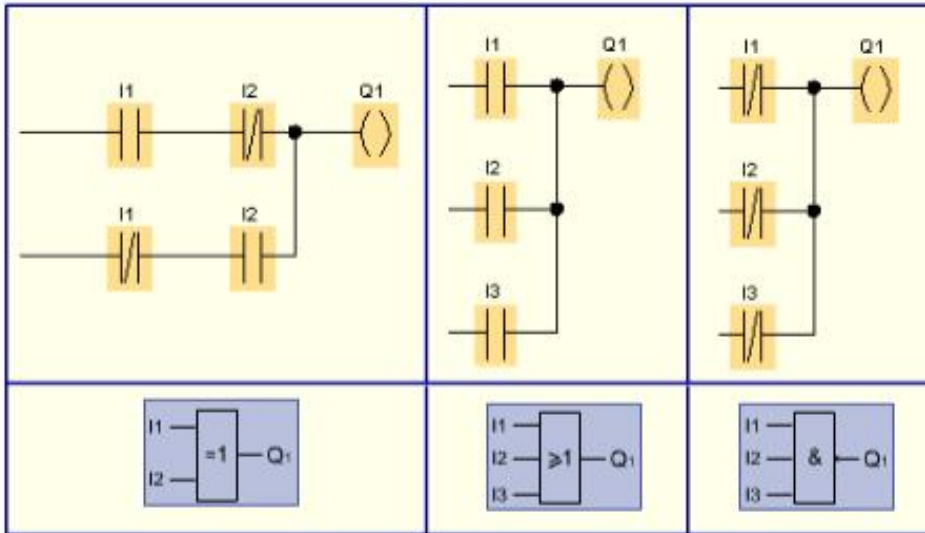

Task 4

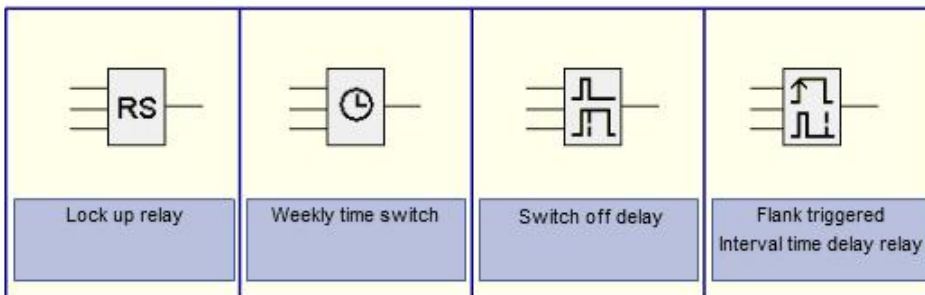


Task 5

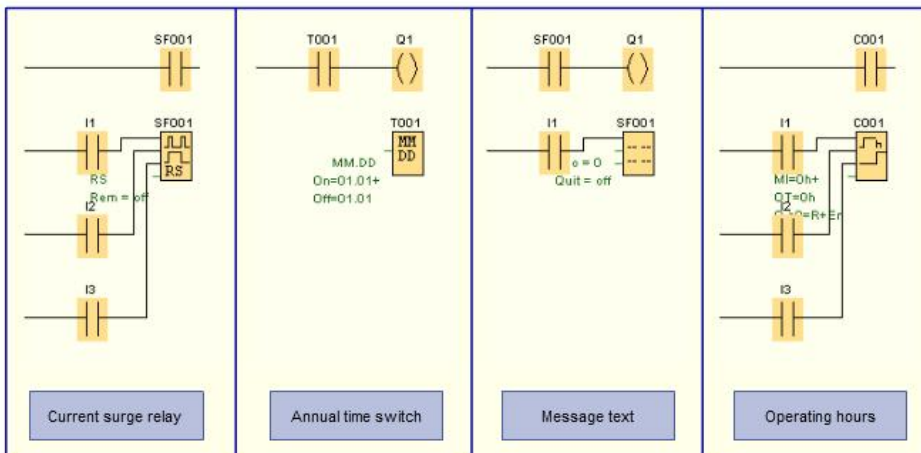

Sample Answers - Practical Assessment:

Task 6:

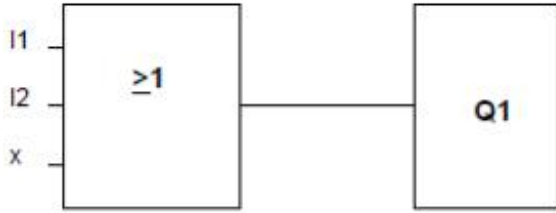

Task 7

